

# Assignment 1

AVVARU BHARAT

**Abstract**—This document shows how to draw logic gates.

Download all latex-tikz codes from

<https://github.com/Bharat437/EE5803-FPGA-LAB/tree/main/Assignment-1>

## 1 PROBLEM

Draw the Logic Circuit for the following Boolean Expression:

$$(X' + Y).Z + W'$$

## 2 EXPLANATION

 


Fig. 1: Logic circuit for  $(X' + Y).Z + W'$